

H26 電力系統の中間試験

NO. 1/4

DATE 2014. 5. 28

171 30

(1)  $V_g = 14.1 \text{ kV} = 10/10 \text{ kV}$

(2)  $\cos \theta_L = \frac{50}{\sqrt{50^2 + 10^2}} = \frac{126}{5} = 0.98$

$\cos \theta_G = \frac{50}{\sqrt{50^2 + (20+10)^2}} = \frac{5}{\sqrt{34}} = 0.857$

(3)  $I = \frac{V_g}{Z_T + Z_L} = \frac{10 \angle 0^\circ}{50 + j30 + j34} = \frac{10 \angle 0^\circ}{50 + j64} = \frac{10 \angle 0^\circ}{\sqrt{34} \angle 51.3^\circ} = \frac{10}{\sqrt{34}} \angle -51.3^\circ \text{ kA}$

$\therefore |I|^2 = \frac{1}{34}$

$S_G = (Z_T + Z_L) |I|^2 = (50 + j30) \frac{1}{34} = 1.47 + j0.882$

1.714

$P_G = 1.47 \text{ MW}, Q_G = 0.882 \text{ MVar}, |S_G| = 1.714 \text{ MVA}$


(4)  $S_L = Z_L |I|^2 = (50 + j10) \frac{1}{34} = 1.47 + j0.294$

$\therefore P_L = 1.47 \text{ MW}, Q_L = 0.294 \text{ MVar}, |S_L| = 1.499 \text{ MVA}$

(1)  $S_B = V_B I_B = 10 \text{ kV} \times 0.2 \text{ kA} = 2 \text{ MVA}$   
 $Z_B = V_B / I_B = \frac{10}{0.2} = 50 \Omega$

(2)  $V_g = \frac{10}{10} = 1.0 \text{ pu}$

$Z_T = \frac{50}{j20} = j0.5 \text{ pu}$

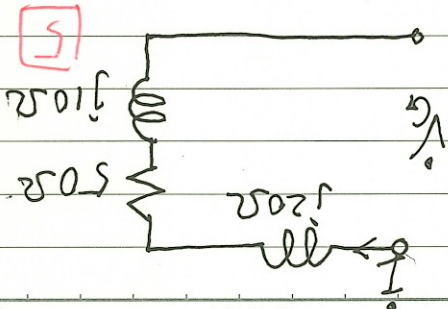

5

15

30

10

5

10

10

10

$$Z_L = \frac{50 + j10}{50} = 1.0 + j0.2 \text{ pu}$$

$$S_G = \frac{1.47 + j0.882}{2} = 0.735 + j0.441 \text{ pu}$$

$$S_L = \frac{1.47 + j0.294}{2} = 0.735 + j0.147 \text{ pu}$$

173 20

(1), (2)

(3) 电压线(复) 必要是也。


理由は

$$I_a + I_b + I_c = 0$$

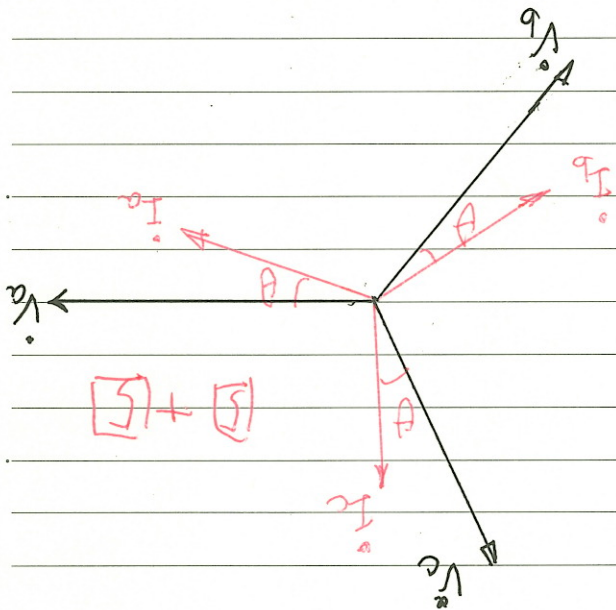(4) 各相が独立に扱える。

理由:

①  $I_a + I_b + I_c = 0$ , ② 各相が独立に扱える, 三相平衡の時



[5] + [5]

[5]

174. 20  
相電圧  $|V| = \frac{\sqrt{3}}{\sqrt{3}} = 1.0 \text{ pu}$ , 相電圧  $S_{1\phi} = \frac{2.1 + j0.6}{3} = 0.7 + j0.2 \text{ pu}$

(1)  $V_p = 1.0 \text{ pu}$ ,  $S_{1\phi} = V_p I_p^*$

$I_p = S_{1\phi}^* = 0.7 - j0.2 \text{ pu}$

[5]

(2) 損失電力

$$P_{\text{loss}} + jQ_{\text{loss}} = Z_p |I_p|^2 = (0.02 + j0.4) \times 0.53 = 0.01 + j0.212$$



[5]

f, 2  $P_{loss} = 0.01 \text{ pu}$ ,  $P_{loss} = 0.212 \text{ pu}$

(3) 受電端 | 送電端 | 相分電力

$$S_{r, \phi} = S_{\phi} - (P_{loss} + jQ_{loss}) = 0.9 + j0.2 - (0.01 + j0.212)$$

$$= 0.69 - j0.012$$

f, 2, 三相電力

$$S_{r, 3\phi} = 3 S_{r, \phi} = 2.07 - j0.036$$

[10]

-1/6, 受電端相電圧  $V_r$  は

$$S_{r, \phi} = V_r I_p^* \rightarrow V_r = \frac{S_{r, \phi}}{I_p^*} \rightarrow |V_r| = \left| \frac{S_{r, \phi}}{I_p} \right|$$

f, 2, 受電端 線間電圧  $V_r$  は

$$|V_r, L-L| = \sqrt{3} |V_r| = \sqrt{3} \times \sqrt{\frac{0.69^2 + j0.012^2}{0.9^2 + 0.2^2}} = 1.842 \text{ pu}$$

[15]

(1) 送電端 | 受電端 | 相分電力

$$\frac{0.2 + j0.8}{1} = \frac{0.2 - j0.8}{0.2^2 + 0.8^2} = 0.294 - j1.176$$

$$\frac{0.1 + j0.5}{1} = \frac{0.1 - j0.5}{0.1^2 + 0.5^2} = 0.364 - j1.923$$

$$\frac{0.1 + j0.4}{1} = \frac{0.1 - j0.4}{0.1^2 + 0.4^2} = 0.588 - j2.353$$



$$I_4 = \frac{0.4}{-0.468 - (-0.483)} = 0.8375 \Rightarrow \textcircled{3} \rightarrow \textcircled{4} : 0.0375 \text{ pu}$$

$$I_3 = \frac{0.5}{-0.051 - (-0.483)} = 0.864 \Rightarrow \textcircled{2} \rightarrow \textcircled{4} : 0.864 \text{ pu}$$

$$I_2 = \frac{0.5}{0 - (-0.468)} = 1.296 \Rightarrow \textcircled{1} \rightarrow \textcircled{3} : 1.296 \text{ pu}$$

$$I_1 = \frac{0.8}{0 - (-0.051)} = 0.064 \Rightarrow \textcircled{2} \rightarrow \textcircled{1} : 0.064 \text{ pu}$$

∴  $\delta_2 = -0.051 \text{ rad}$ ,  $\delta_3 = -0.468 \text{ rad}$ ,  $\delta_4 = -0.483 \text{ rad}$

$V_4 = -0.483$

~~$V_3 = -4.995$ ,  $V_4 = -2.575$ ,  $V_3 = -0.468$~~


(1)  $V_3 = -(0.5 + 0.625 V_2)$  (4)

(2)  $V_4 = -0.4 + 1.625 V_2$  (5)

$$-0.9 = \frac{V_3 - 0}{V_3 - V_4} + \frac{0.5}{V_3 - V_4} \quad (3)$$

$$0.8 = \frac{V_2 - 0}{V_2 - V_4} + \frac{0.8}{V_2 - V_4} \quad (2)$$
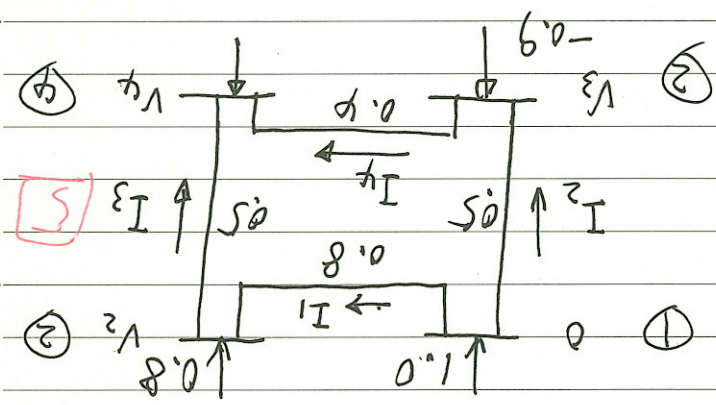
$$1.0 = \frac{0 - V_2}{0 - V_3} + \frac{0.8}{0 - V_3} \quad (1)$$



$$Y = \begin{bmatrix} 0.658 - j3.099 & -0.294 + j1.196 & -0.364 + j1.923 & 0 \\ 0.658 - j3.099 & 0 & 0 & -0.364 + j1.923 \\ 0.952 - j4.276 & 0.952 - j4.276 & -0.588 + j2.353 & 0.952 - j4.276 \\ * & * & * & * \end{bmatrix}$$